
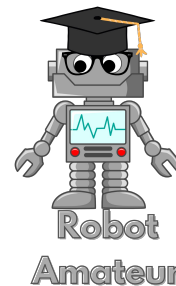


Standalone Test Diagram

Wiring Connections

PIR: Vcc	Arduino: 5V
PIR: Ground	Arduino: Ground
PIR: Output	LED: Longueur leg
Resistor	LED: Shorter leg
Resistor	Arduino: Ground

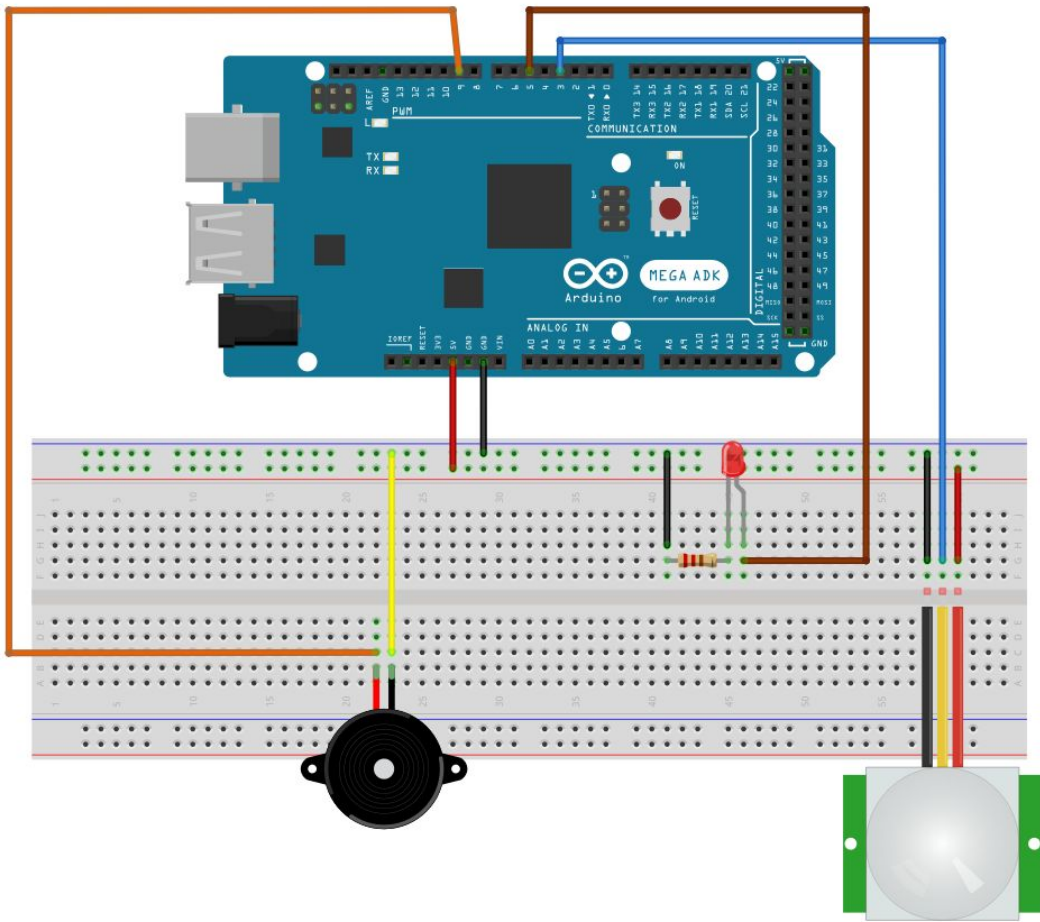



Home Security Alarm Test Diagram

New Wiring Connections

LED: Longueur leg	Arduino: Digital IO 5
Buzzer: +	Arduino: Digital IO 9
Buzzer: -	Arduino: Ground
PIR: Output	Arduino: Digital IO 3

Old Wiring Connections

PIR: Vcc	Arduino: 5V
PIR: Ground	Arduino: Ground
Resistor	LED: Shorter leg
Resistor	Arduino: Ground

